

EVP DEC = 18V2 = 25,46 VP Vimox = 25,46 = 0,56 = 24,90V Vimin = 6+3 = 9V Vand = 24,9 - 9 = 15,190V © VPSEC= 22 V2 = 31,11 VP Vimox = 31,11-0,6 = 30,51 V Vimin = 18+3 = 21V Vord= 30,51-21= 9,51V BVpsec = 2213 = 31,11 Vp Vimox = 31,11 -0,65 = 30,46 V Vimin = 12+3=15 Vord = 30, 46-15=15,46 V Imox = 1,26 = 105mA C = 105m = 113,18 UF 10

@ Vpsec=-24V2=-33,944/4 Vimox=-33,94+0,72=-33,02V Vimin=-12-3=-15V Vand=-33,02-(-16)=-18,02V Veap=-33,02-(-18,02/2)=[-24,11V] © Vp.20c=-03√2 =-30,53 Vp Vimox = -32,53 +046=-31,89V Vimin=-5-3=-8V Vard=-31,84-(-8)=-23,84V Vcop=-31,84-(-2384/2)=[-19,93√]

(1) Vp 12 = -19 V2 = -26 8 4 Vp Vimox = -26,87 + 0,49 = -26,13 V Vimin = -12-3 = -15 V Vond = -26,13 -(-15) = [-11,13 V]